

59

where:

$$\tau = \frac{10 V_{pk}}{R_1 + 12.2}$$


$$\text{duty cycle (\%)} = \frac{100}{1 + \tau} \quad (\%)$$

cycle of the pulse train. Resistor R_1 also limits the output current of op amp A_3 . If the amplitudes of the square and pulse waves are different from those indicated here, the circuit equations must be modified.

To calculate the circuit parameters, first choose resistor R_1 to obtain the duty cycle desired. Next, fix either R or C (preferably the latter), and calculate the other parameters to obtain the desired frequency. The resistor values should be large enough to avoid loading the dividers, but not so high that bias current causes excessive offset.

*Juan R. Pimentel, Research Engineer, Dept. of
Electrical Engineering, University of Virginia,
Charlottesville, VA 22901* CIRCLE NO. 312

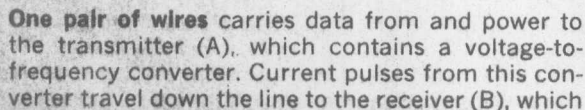For the interface between the transducer and the twisted-pair transmission line, the transmitter uses a low-cost IC voltage-to-frequency (v/f) converter. The converter generates a train of current pulses with a frequency proportional to the transducer's output voltage; accuracy is 1% or better.



converts them to TTL levels. Transistor Q_1 provides low-impedance power to the transmitter, while passing current pulses from the transmitter to R_s , which converts them into voltage pulses.

In the receiver, these pulses are converted to TTL levels for subsequent processing. In addition to converting levels, the receiver sends constant-voltage power to the transmitter from a low-impedance stabilizer. Low output impedance ensures high common-mode rejection and excellent noise immunity.

With the circuit values shown in the figure, the transmitter (A) has an output frequency range of 0 to 10 kHz. Other ranges require changing current-setting resistor R_s and timing resistor R_b , as well as capacitors C_o , C_b and C_s (see table). Adding an input op amp improves the transmitter's accuracy to 0.05%.

In the transmitter, diode D_f isolates the transducer and converter from effects of the output current pulses. During each pulse, this diode blocks, and capacitor C_f supplies power to the local circuits.

The receiver (B) has two sections, one serving as a stabilizer that also converts the returning current pulses to a voltage, and one serving as a gain stage and level setter. The stabilizer uses the +15-V supply for its reference, so its stability depends on that of the supply.

Power to the transmitter comes from transistor Q_1 , an emitter-follower current booster in the stabilizer. Resistor R_s is a collector load, which converts the current pulses from the transmitter into voltage pulses. Transistor Q_1 operates simultaneously as an emitter follower, to provide a stable voltage, and as a common-base amplifier for the incoming current pulses.

The remaining circuitry clips and amplifies the pulses from R_s to convert them to TTL levels having a rise time of about 2.5 μ s. The RC4559 is used for its relatively fast response. Diode D_1 clips negative excursions to ensure that the output op amp does not generate large negative outputs. The output is set to TTL levels by the feedback network made up of diodes D_2 and D_3 and the resistor string, R_1 through R_4 .

The op amp's output, which has a fanout of about 15, has a HIGH output level that varies with the pulse repetition rate. The lowest value (+3.7 V) of this level corresponds to a rate of 100 kHz and a width of 5 μ s.

The transmitter, or source impedance, and the receiver, or load impedance, need not match the cable impedance. The receiver looks like a short to the

Operating range	C_o	C_b	C_s
0 to 1 kHz	0.1 μ F	10 μ F	1 μ F
0 to 10 kHz	10 nF	1 μ F	0.1 μ F
0 to 100 kHz	1 nF	0.1 μ F	10 nF

transmission line, so a transmitted pulse is inverted when it is reflected. Diode D_f at the transmitter absorbs the positive reflection to prevent any further reflection back to the receiver.

The transmitter's output pulse width is approximately 1.1 ($R_o C_o$), which is 75 μ s for the values shown. The scale factor is

$$\frac{F_o}{V_{in}} = \frac{R_s}{T R_b V_{ref}}$$

where F_o is the output frequency and V_{ref} is 2.25 V. The output current pulse is

$$I_p = \frac{V_r - 0.3}{R_L + 2 R_t}$$

where R_t is the resistance of one conductor of the twisted pair, calculated from its resistance per foot.

Noise filtering in the receiver can be tailored to cope with electromagnetic interference from such sources as motors and power lines, without degrading performance. Capacitor C_m controls the response time of the regulator, and the $R_a C_a$ network forms a low-pass filter for the output stage.

For a 75- μ s pulse width, typical values are 5 nF for C_m , 1 nF for C_a , and 1 k Ω for R_a . In terms of the transmitter's timing components,

$$R_a C_a \approx \frac{R_o C_o}{20} \quad \text{and} \quad C_m \approx \frac{R_o C_o}{4 R_m}$$

Finally, the sensitivity control should be adjusted for proper output levels and minimum pulse jitter.

S. Fred Dabney, Senior Linear Applications Engineer, Raytheon Semiconductor, 350 Ellis St., Mountain View, CA 94042.

CIRCLE NO. 313

IFD Winner for February 1, 1979

Bob Ferguson, Systems Engineer, Computer/Federal Systems Engineering, Motorola Semiconductor, M/S Z315, 5005 E. McDowell Rd., Phoenix, AZ 85008. His idea "Simple Protective Circuit Ensures Proper Power Sequence to MOS RAMs" has been voted the most valuable of Issue Award.

Vote for the Best Idea in this issue by circling the number of your selection on the Reader Service Card at the back of this issue.

SEND US YOUR IDEAS FOR DESIGN. You may win a grand total of \$1050. Here's how. Submit your IFD describing a new and important circuit or design technique, the clever use of a new component or test equipment, packaging tips, cost-saving ideas to our Ideas for Design editor. Ideas can only be considered for publication if they are submitted exclusively to ELECTRONIC DESIGN. You will receive \$20 for each published idea, \$30 more if it is voted best of issue by our readers. The best-of-issue winners become eligible for the Idea of the Year award of \$1000.

ELECTRONIC DESIGN cannot assume responsibility for circuits shown nor represent freedom from patent infringement.